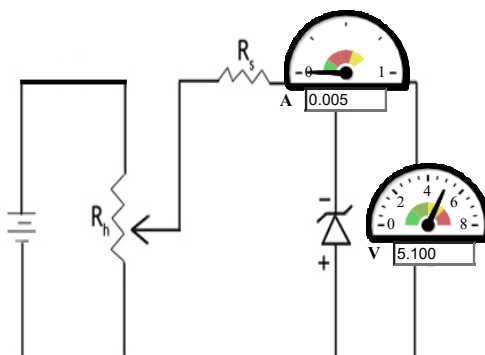


## Zener characteristics

### INSTRUCTION

#### EXPERIMENTAL TABLE

Serial No.	Zener Voltage(Volt)	Current(mAmp)
1	0.120	0.000
2	1.297	0.000
3	2.360	0.001
4	3.362	0.002
5	4.341	0.003
6	5.100	0.005



#### CONTROLS

Select Diode: IN4733A

$R_h$  :  ohms

Add to Table


Plot

Clear

Print It

#### GRAPH PLOT

#### V-I Plot

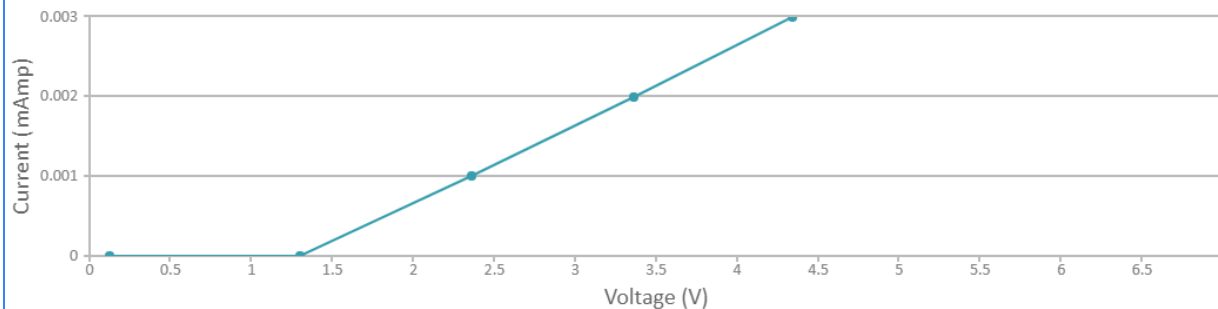



## V-I Characteristics of Zener Diode

Scale:-

X-axis:- 1 unit = 1 V

Y-axis:- 1 unit = 0.001 mA

