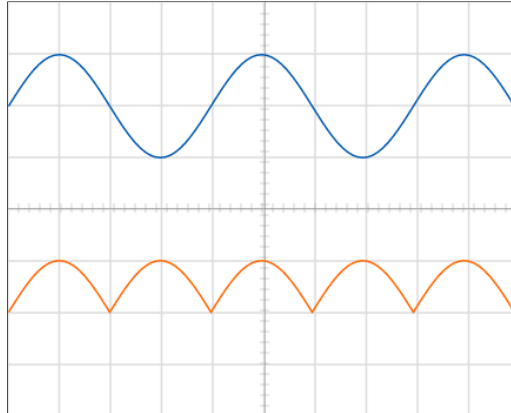


## Full Wave Rectifier

### INSTRUCTION

#### OSCILLOSCOPE



Channel 1 Channel 2 Ground Dual

**2500**  
Frequency(Hz)

**1**  
Amplitude(Volt)

Off

#### CALCULATION




$$V_{rms} = \frac{V_m}{\sqrt{2}}, V_m \text{ is the peak voltage}$$

$$V_{dc} = \frac{2 \times V_m}{\pi}$$


$$\text{Ripple Factor} = \frac{V_{ac}}{V_{dc}} \quad \text{Since, } V_{ac} = \sqrt{(V_{rms}^2 - V_{dc}^2)}$$

Peak Current: 2.9999999892691407 mA

### CIRCUIT

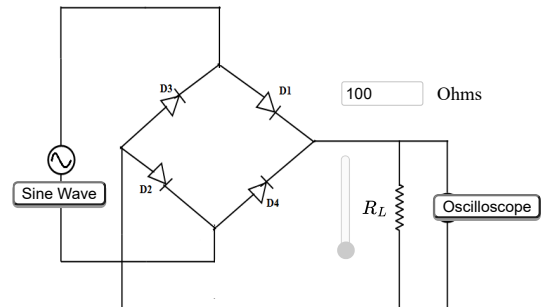


### CONTROLS

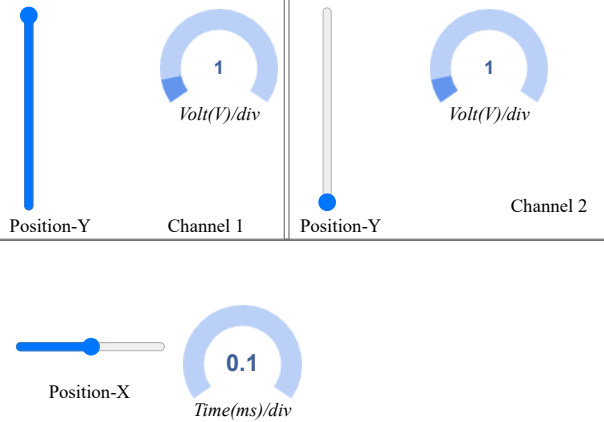

## Full Wave Rectifier

### INSTRUCTION

#### OSCILLOSCOPE

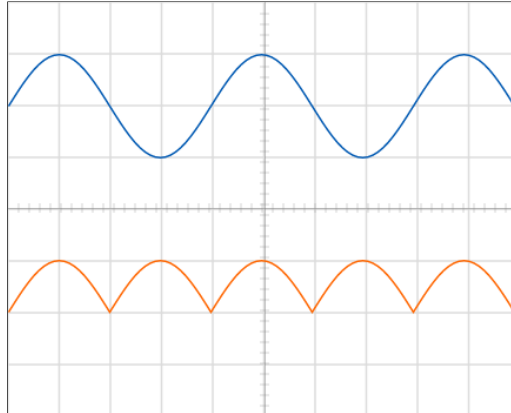

Channel 1 Channel 2 Ground Dual

**2500**  
Frequency(Hz)

**1**  
Amplitude(Volt)

#### CALCULATION




$$V_{rms} = \frac{V_m}{\sqrt{2}}, V_m \text{ is the peak voltage}$$

$$V_{dc} = \frac{2 \times V_m}{\pi}$$


$$\text{Ripple Factor} = \frac{V_{ac}}{V_{dc}} \quad \text{Since, } V_{ac} = \sqrt{(V_{rms}^2 - V_{dc}^2)}$$

Peak Current: 2.9999999892691407 mA

#### CIRCUIT

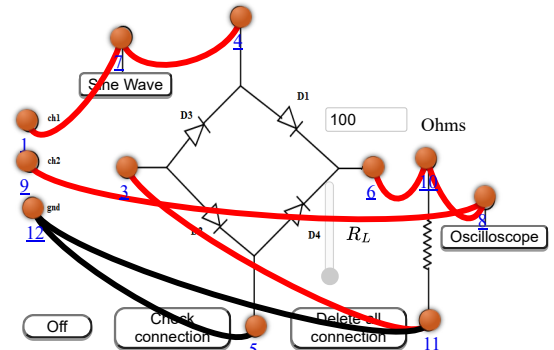

#### CONTROLS

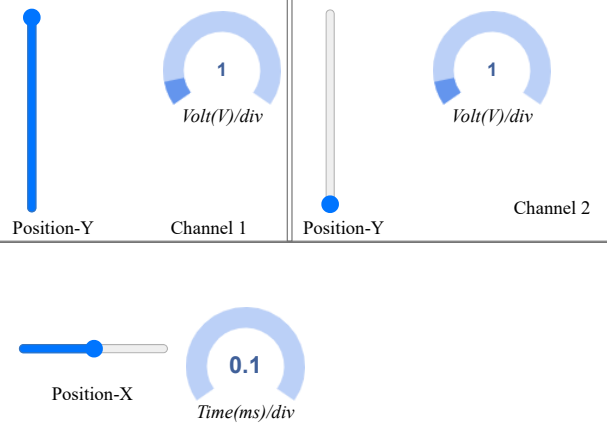





## Full wave Rectifier

Scale:-

X-axis:- 1 unit = 0.1 ms/div

Y-axis:- 1 unit = 1 Volt/div

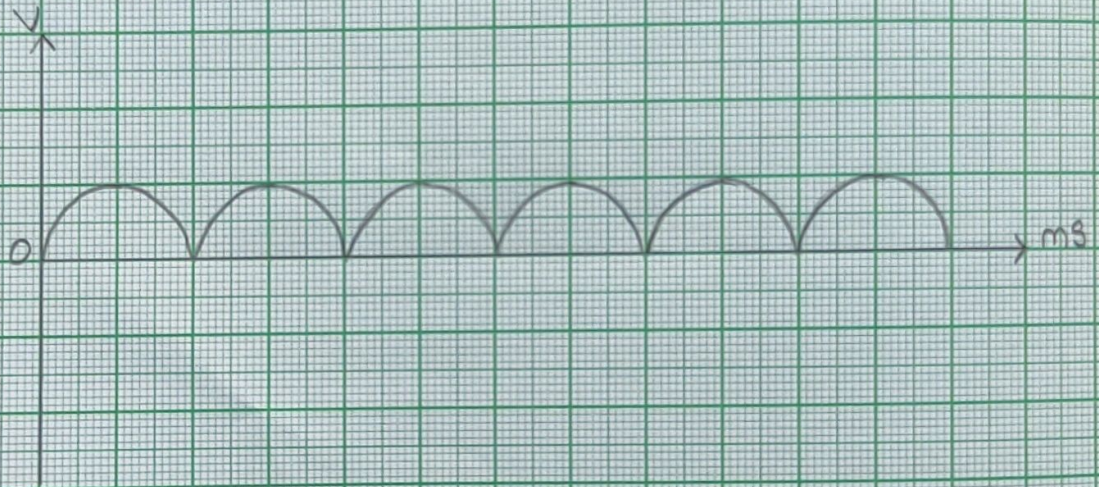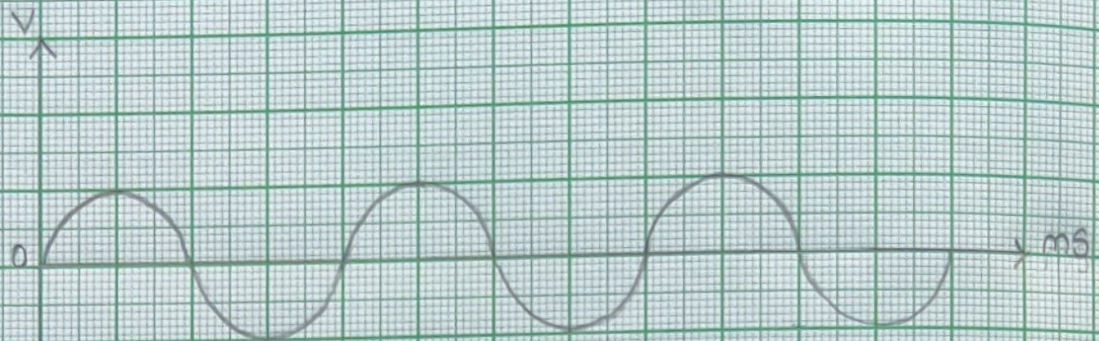



# Full wave Rectifier

## Calculation

$$\text{Peak voltage } (V_m) = 1V$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$= \frac{1}{\sqrt{2}}$$

$$= 0.707 V$$

$$V_{dc} = \frac{2 \times V_m}{\pi}$$

$$= \frac{2 \times 1}{\pi}$$

$$= 0.6366 V$$

$$V_{ac} = \sqrt{(V_{rms})^2 - (V_{dc})^2}$$

$$= \sqrt{(0.707)^2 - (0.6366)^2}$$

$$= 0.3075 V$$

$$\text{Ripple factor} = \frac{V_{ac}}{V_{dc}}$$

$$= \frac{0.3075}{0.6366}$$

$$= 0.48303$$

$$\text{Therefore, Ripple factor} = 0.483$$